



ELEE 2790U: Electric Circuit

CRN: 73165 02:10 PM - 03:30 PM Tuesday - SIRC 2020

CRN: 73166 03:40 PM - 05:00 PM Friday - UP1502

Tutorial 8 ELEE 2790U

Ahmad Mousa & Victor Ijeh

Email: Ahmad.mousa@ontariotech.net & victor.ijeh@ontariotechu.ca

Winter, 2023

Problem 1

Given that $V_{bn} = 110 \angle 30^\circ \text{ V}$, find V_{an} and V_{cn} , assuming a positive (*abc*) sequence.

$$V_{bn} = 110 \angle 30^\circ$$

$$V_{an} = 110 \angle 30^\circ + 120^\circ \Rightarrow 150^\circ$$

$$V_{cn} = 110 \angle 30^\circ - 120^\circ \Rightarrow -90^\circ$$



sol

$$I_{AB} = \frac{V_{AB}}{Z_A}$$

$$I_A = \sqrt{3} I_{AB}$$

$$I_{BC} = I_{AB} \angle \phi - 120^\circ$$

$$I_{CA} = I_{AB} \angle \phi + 120^\circ$$



Problem 2

A positive-sequence, balanced Δ -connected source supplies a balanced Δ -connected load. If the impedance per phase of the load is $18 + j12 \Omega$ and $I_a = 9.609 \angle 35^\circ$ A, find I_{AB} and V_{AB} .

————— Z

$$I_{AB} = \frac{I_a 9.609 \angle 35^\circ}{\sqrt{3}} \angle 30^\circ \Rightarrow 5.548 \angle 65^\circ$$

$$I_{AB} = \frac{V_{AB}}{Z_A}$$

sol

$$Z = 18 + j12 = 21.63 \angle 33.69^\circ$$

$$V_{AB} = I_{AB} Z = 5.548 \angle 65^\circ \cdot 21.63 \angle 33.69^\circ$$

$$V_{AB} = 120 \angle 98.69^\circ$$



Sol



Problem 3

Calculate the line current required for a 30-kW three-phase motor having a power factor of 0.85 lagging if it is connected to a balanced source with a line voltage of 440 V.

650

$$P = S \cos \phi \Rightarrow S = \frac{P}{\cos \phi} = \frac{30 \times 10^3}{0.85} = 35.29 \text{ kVA}$$

$$S = \sqrt{3} V_L I_L$$

$$35.29k \text{ VA} = \sqrt{3} \text{ VL IL}$$

$$35.29k \text{ VA} = \sqrt{3} \times 440 \times \text{IL}$$

$$46.31 \text{ A}$$